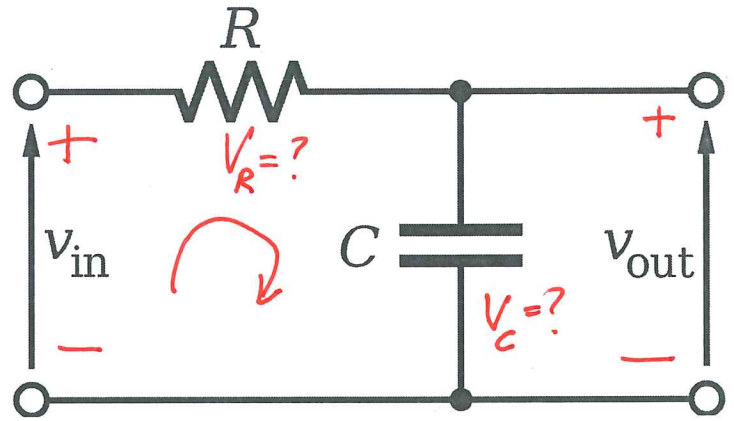


## Low Pass Filter with a cut-off:

Given a voltage @ input

Step or continuous wave.



For Resistor Load. Ohm's Law  $V = IR$

$$V_R = I_R R$$

Across Capacitor Current  $I = C \frac{dv}{dt}$ .

$V_C$  across Capacitor

$$\therefore I_C = C \frac{dv_C}{dt}$$

using Voltage Law  $V_R \rightarrow$  Resistor,  $V_C \rightarrow$  Capacitor

$$I_R = I_C \quad \text{and} \quad V_{in} = V_R + V_C$$

$$\frac{V_R}{R} = C \frac{dv_C}{dt} \quad \text{and using } \uparrow V_R = V_{in} - V_C$$

sub

$$\frac{V_{in} - V_C}{R} = C \frac{dv_C}{dt} \quad ; \quad \text{taking } -\frac{V_C}{R} \text{ to right.}$$

$$C \frac{dv_C}{dt} + \frac{V_C}{R} = \frac{V_{in}}{R}$$


$$\frac{dv_C}{dt} + \frac{V_C}{RC} = \frac{V_{in}}{RC} \quad ; \quad \text{But } V_C = V_{out}$$

$$\boxed{\frac{dv_o}{dt} + \frac{1}{RC} v_o = \frac{1}{RC} V_{in}}$$

Let's say  $V_{in} = V^* \sin \omega t$  

$$V_o = A \cos \omega t + B \sin \omega t.$$


$$= -\frac{wRC}{1+(wRC)^2} V^* \cos \omega t + \frac{1}{1+(wRC)^2} V^* \sin \omega t$$

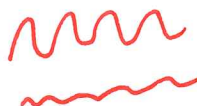Look @ Magnitude of output. 



$$|V_{out}| = \frac{1}{1+w^2(RC)^2} V^* = \frac{1}{1+w^2(RC)^2} |V_{in}|$$





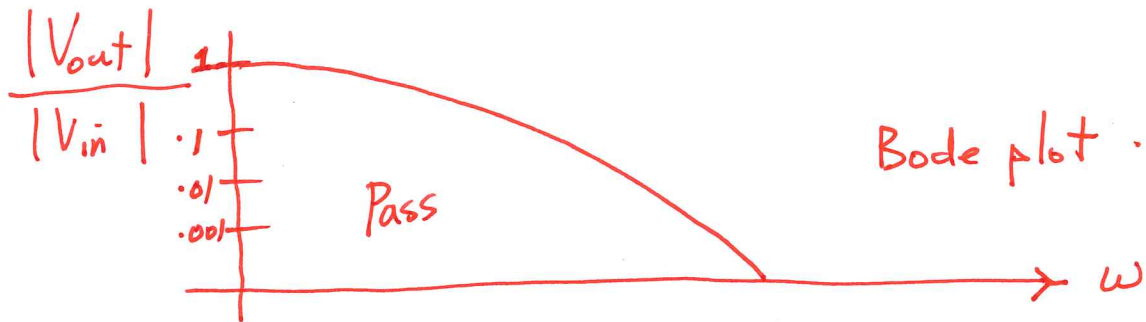



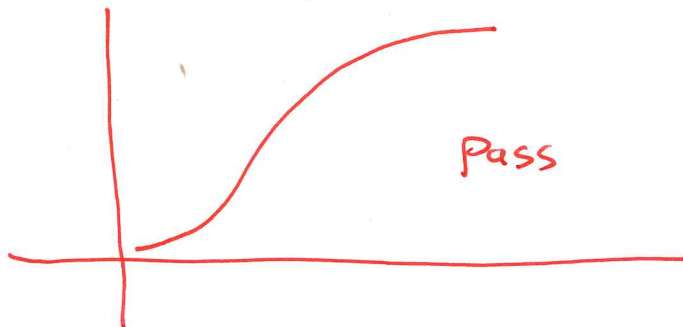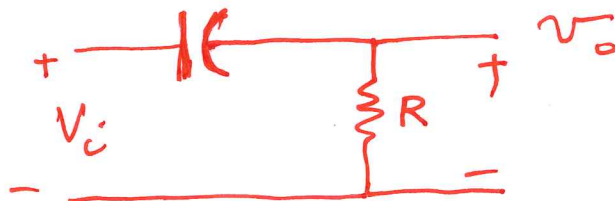

Also write:  
 $\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{s+1}}$

check  $w$  is small ;  $V_o$  is almost 1.  
 $w$  is high ;  $V_o$  is almost  $\phi$ .



High Pass:




LPF	HPF
	
	
	
	
	
BPF	BSF

What if you applied a Step Function to this filter?

What

would

$V_o$  look like?

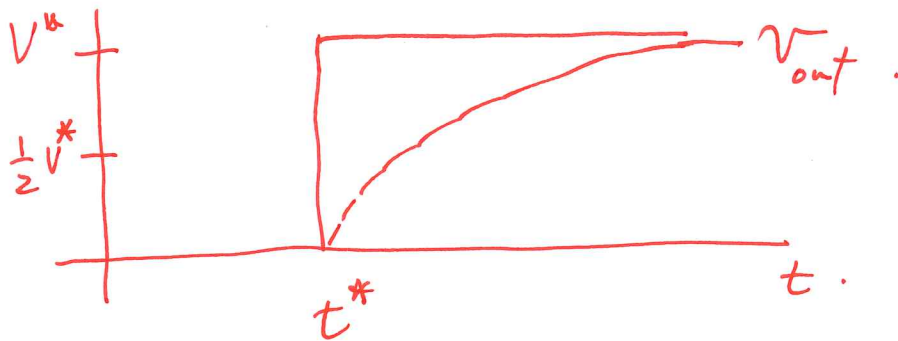


$$V_o = V^* \left[ 1 - e^{-\frac{1}{RC}(t-t^*)} \right]$$

If we wanted to see how long it took to get to  $\frac{1}{2} V^*$ , we do the following.

$$V_o = V^* \left[ 1 - e^{-\frac{1}{RC}(t-t^*)} \right] = \frac{1}{2} \Rightarrow e^{-\frac{1}{RC}(t-t^*)}$$

$$\therefore t - t^* = -RC \ln\left(\frac{1}{2}\right) = 0.693 \text{ (RC)}$$

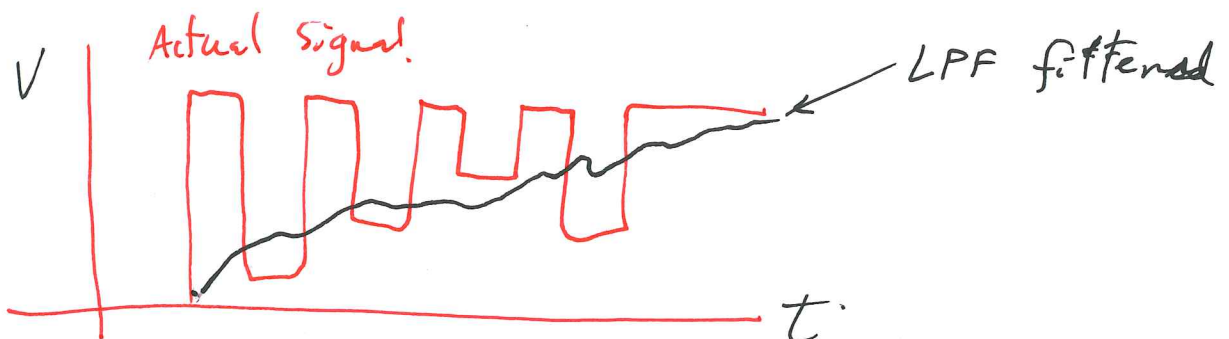If RC gets larger system responds slower  
 RC " smaller " " faster.



## Bridge Circuits:

Bridge circuits are used to make a form of measurement:

- Change in resistance
- Change in inductance
- Change in capacitance
- Oscillating frequency

DC. Bridge - All Resistors

AC. Bridge - Impedances

- \* Bridge is balanced iff
- (A) show no current flow
- \* when balanced

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad ; \quad \text{For Any } R_L$$

$$\text{look @ } V_o = V_A - V_B \cdot V_A$$


$$= \frac{R_1}{R_1 + R_2} V_{ref} - \frac{R_3}{R_3 + R_4} V_{ref}$$

$$= V_{ref} \left( \frac{R_1 R_3 + R_1 R_4 - R_3 R_1 - R_3 R_2}{(R_1 + R_2)(R_3 + R_4)} \right) = \frac{R_1 R_4 - R_3 R_2}{(R_1 + R_2)(R_3 + R_4)} V_{ref}$$

Assume  $R_1 = R_2 = R_3 = R_4 = R$ .  $\therefore$  Bridge is balanced.  $\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$

Let's increase  $R_1$  by  $\Delta R$ , all others @  $R$

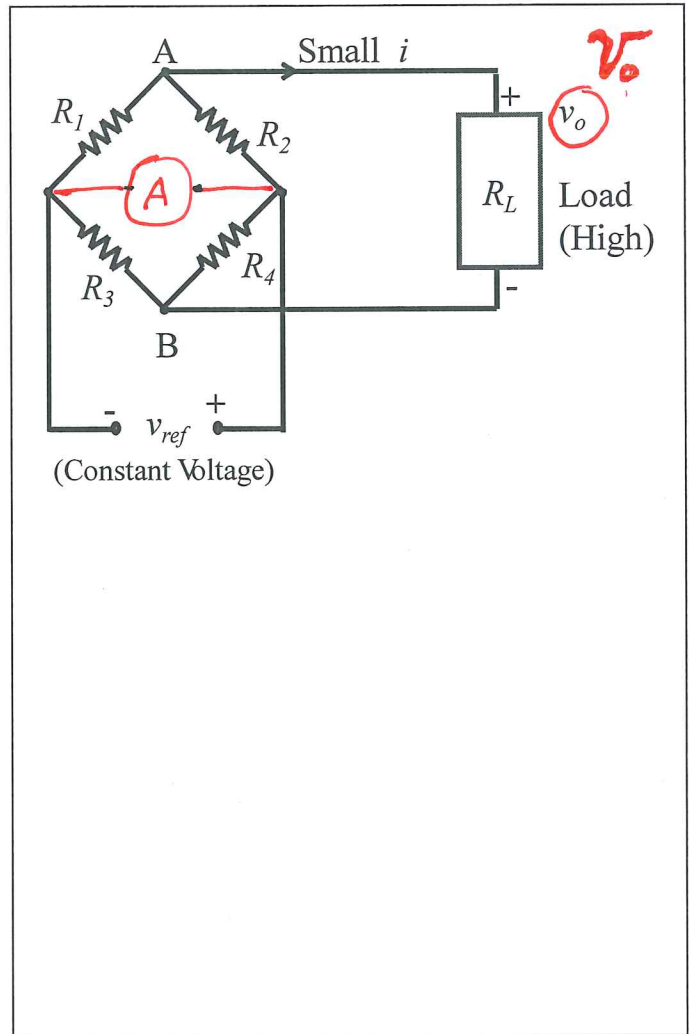$R \Rightarrow$  The only Active strain gage.



Continuing.

①

$$\delta V_o = \frac{[(R + \delta R)R - R^2]}{(R + \delta R + R)(R + R)} \quad v_{ref} - 0 \quad \uparrow$$


When Balanced

$$\frac{\delta V_o}{V_{Ref}} = \frac{R^2 + R\delta R - R^2}{4R^2 + 2R\delta R}$$

$$= \frac{R\delta R}{4R^2 + 2R\delta R}$$

$$= \frac{\delta R}{4R + 2\delta R}$$
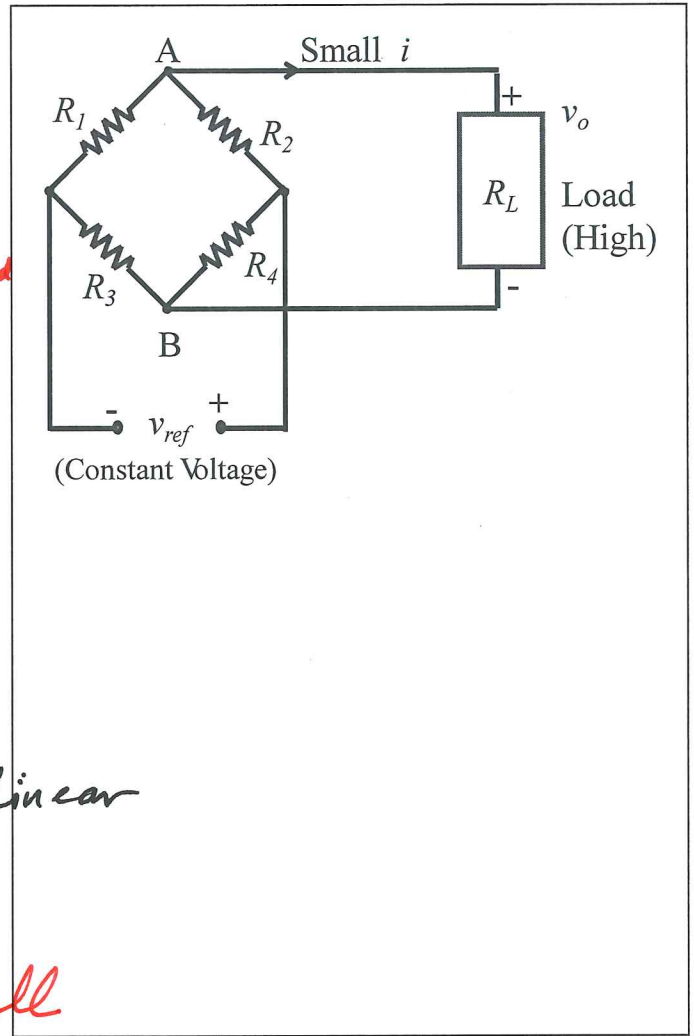
$$= \frac{\delta R/R}{4 + 2\delta R/R}; \quad \frac{\delta R}{R} : \text{Non Linear}$$



If we assume  $\frac{\delta R}{R}$  is very small compared to 2; we get linearized relation.

$$\frac{\delta V_o}{V_{Ref}} = \frac{\delta R}{4R}; \quad \frac{1}{4} \Rightarrow \text{Bridge Sensitivity} \quad \left[ \begin{array}{l} \text{Active} \\ \text{Resistance} \\ R \rightarrow R + \delta R \end{array} \right]$$

$\Rightarrow$  Bridge sensitivity is given by  $\frac{\delta V_o}{\delta R}$


$$\therefore \frac{\delta V_o}{\delta R} = \frac{V_{ref}}{4R} \quad \text{--- (2)}$$

$$N_p (\text{Non-linearity } \%) = 100 \left( 1 - \frac{\text{Linearized output}}{\text{Actual output}} \right) \%$$

From Eq. ① + ②  $N_p = 50 \left( \frac{\delta R}{R} \right) \%$
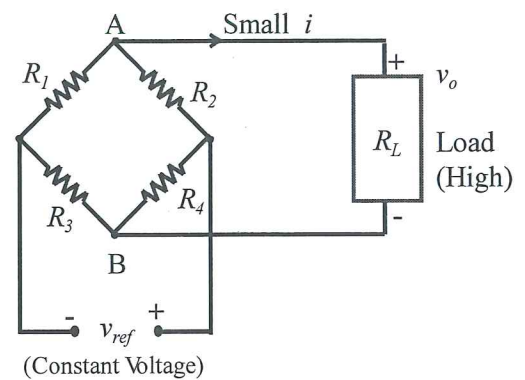
### Example:

Suppose that in Figure on the right, at first  $R_1 = R_2 = R_3 = R_4$ . Now increase  $R_1$  by  $\delta R$ , decrease  $R_2$  by  $\delta R$ . This will represent two active elements that act in reverse, as in the case of two strain gage elements mounted on the top and the bottom surfaces of a beam in bending. Show that the bridge output is linear in  $\delta R$  in this case.



### Solution:

$$R_1 = R + \delta R, R_2 = R - \delta R$$


$$v_o = v_A - v_B = \frac{R + \delta R}{(R + \delta R) + (R + \delta R)} v_{ref} - \frac{R}{R + R} v_{ref}$$

$$\delta v_o = \frac{(R + \delta R) 2R - R(R + \delta R)(R - \delta R)}{(2R)(2R)} v_{ref}$$

$$\approx v_o = \frac{2R^2 + 2\delta R - R(R^2 - (\delta R)^2)}{4R^2} v_{ref}$$

=
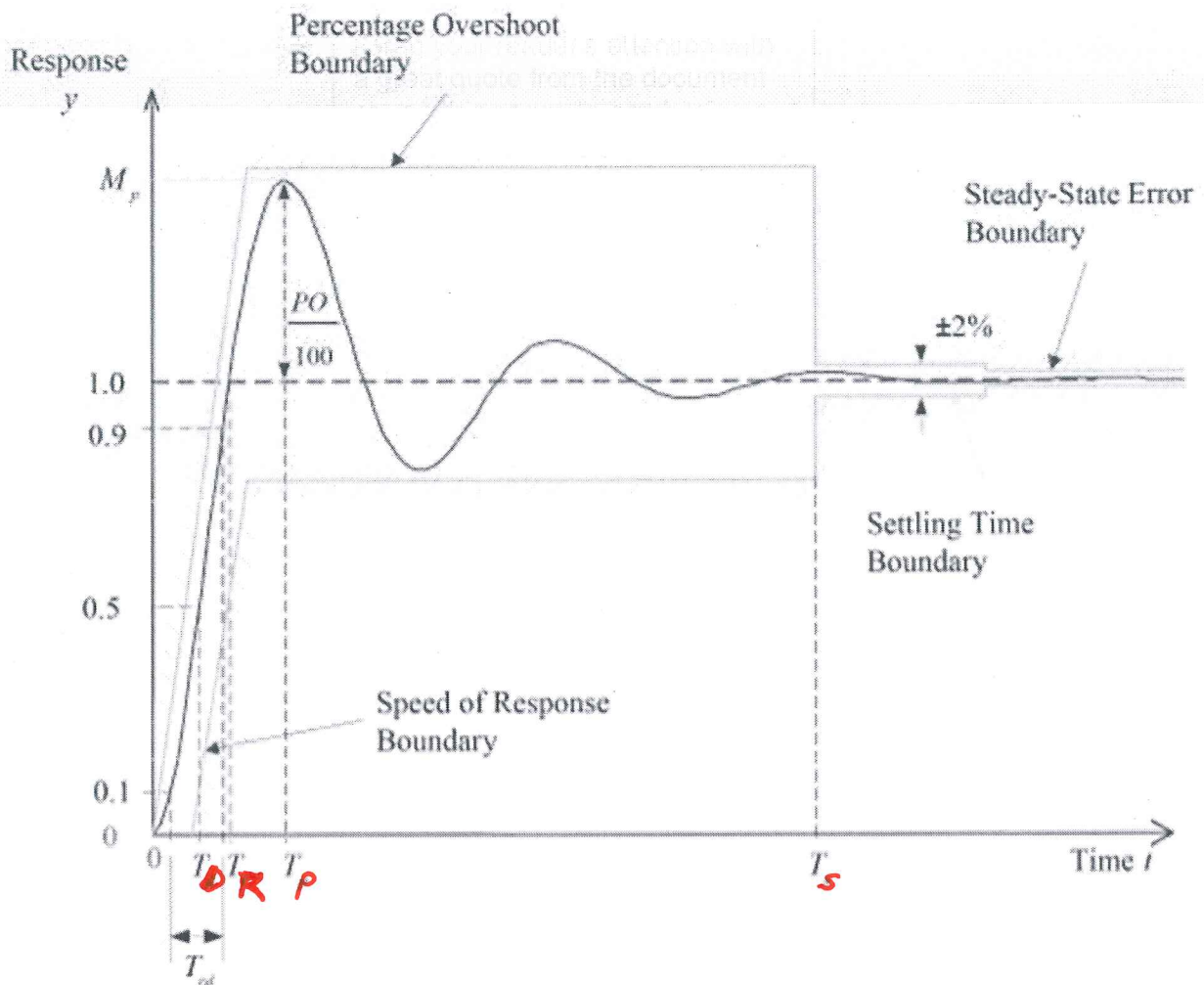
$$\frac{\delta v_o}{v_{ref}} = \frac{\delta R}{2R} \quad ; \quad \cdot 0.5 \%$$



Rise Time [ $T_r$ ]: Time needed to pass 90% of steady state value, first time.

Delay Time [ $T_d$ ]: Time needed to pass 50% of " " " "

Peak Time [ $T_p$ ]: Time for first peak.

Settling Time [ $T_s$ ]: Time that the signal reaches  $\pm 2\%$  of steady state value and remains there.