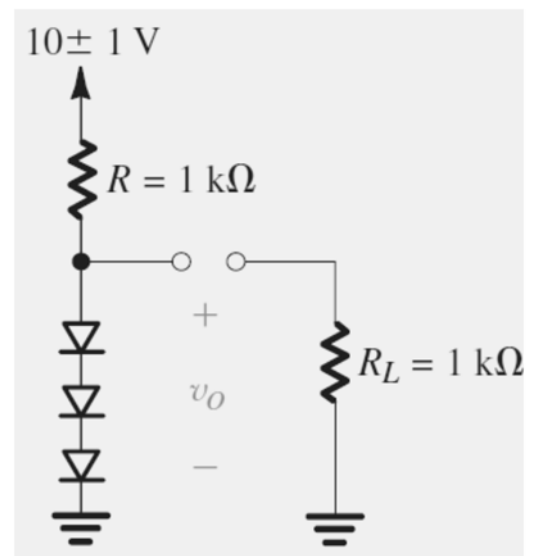





## 8. Use of the Diode Forward Drop in Voltage Regulation:

- An application is the use of diodes to create a regulated voltage.
  - A **voltage regulator** is a circuit whose purpose is to provide a constant dc voltage between its output terminals. The output voltage is required to remain as constant as possible in spite of:
    - a) Changes in the load current drawn from the regulator output terminal and
    - b) Changes in the dc power-supply voltage that feeds the regulator circuit.Since the forward-voltage drop of the diode remains almost constant at approximately 0.7 V while the current through it varies by relatively large amounts, a forward-biased diode can make a simple voltage regulator.

Consider the circuit shown in Fig. 4.17. A string of three diodes is used to provide a constant voltage of about 2.1 V. We want to calculate the percentage change in this regulated voltage caused by (a) a  $\pm 10\%$  change in the power-supply voltage, and (b) connection of a 1-k $\Omega$  load resistance.


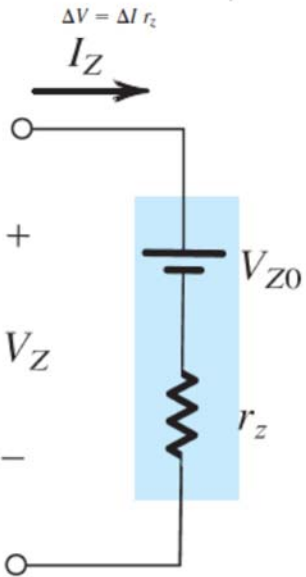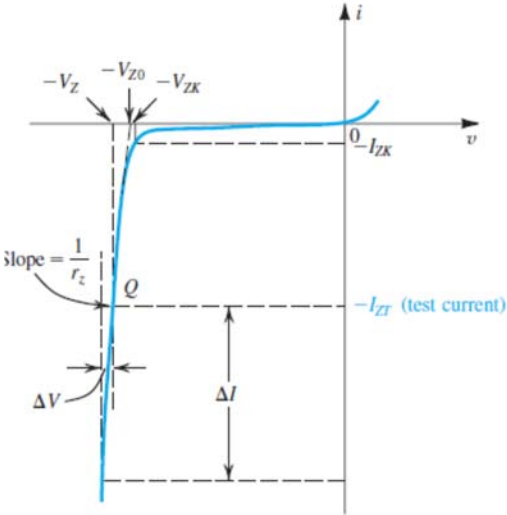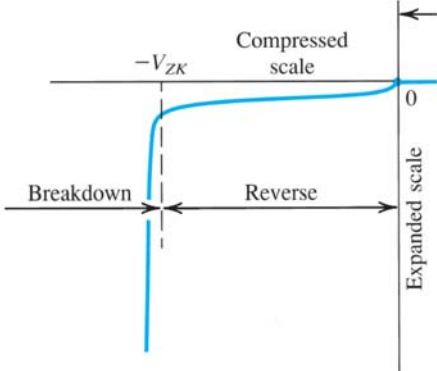
# Operation in the Reverse Breakdown Region—Zener Diodes:




## Temperature Effects:

- The dependence of the Zener voltage  $V_Z$  on temperature is specified in terms of its **temperature coefficient TC**, or **temco** as it is commonly known, which is usually expressed in  $\text{mV}/^\circ\text{C}$ .
- The value of TC depends on the Zener voltage, and for a given diode the TC varies with the operating current.
- Zener diodes whose  $V_Z$  are lower than about 5 V exhibit a negative TC.
- On the other hand, Zeners with higher voltages exhibit a positive TC.
- The TC of a Zener diode with a  $V_Z$  of about 5 V can be made zero by operating the diode at a specified current.
- Another commonly used technique for obtaining a reference voltage with low temperature coefficient is to connect a Zener diode with a positive temperature coefficient of about  $2 \text{ mV}/^\circ\text{C}$  in series with a forward-conducting diode.
- Since the forward-conducting diode has a voltage drop of  $\approx 0.7 \text{ V}$  and a TC of about  $-2 \text{ mV}/^\circ\text{C}$ , the series combination will provide a voltage of  $(V_Z + 0.7)$  with a TC of about zero.


**4.16** A zener diode whose nominal voltage is 10 V at 10 mA has an incremental resistance of  $50 \Omega$ . What voltage do you expect if the diode current is halved? Doubled? What is the value of  $V_{Z0}$  in the zener model?

**4.17** A zener diode exhibits a constant voltage of 5.6 V for currents greater than five times the knee current.  $I_{ZK}$  is specified to be 1 mA. The zener is to be used in the design of a shunt regulator fed from a 15-V supply. The load current varies over the range of 0 mA to 15 mA. Find a suitable value for the resistor  $R$ . What is the maximum power dissipation of the zener diode?

## Rectifier Circuits:



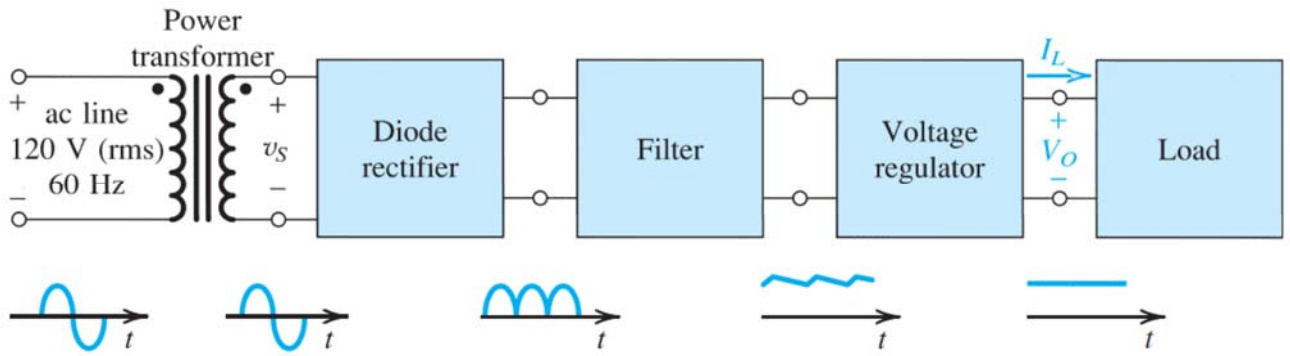


## The Half-Wave Rectifier:

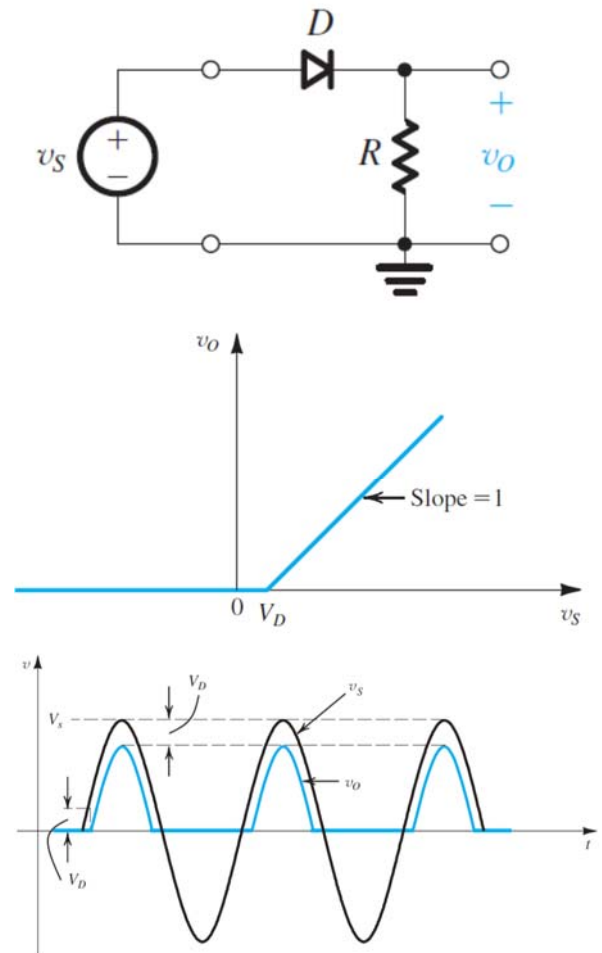

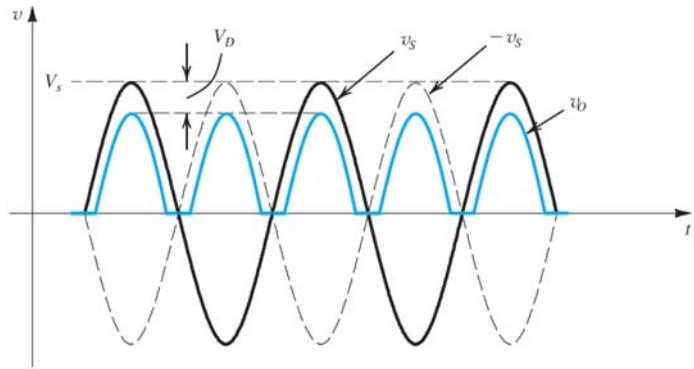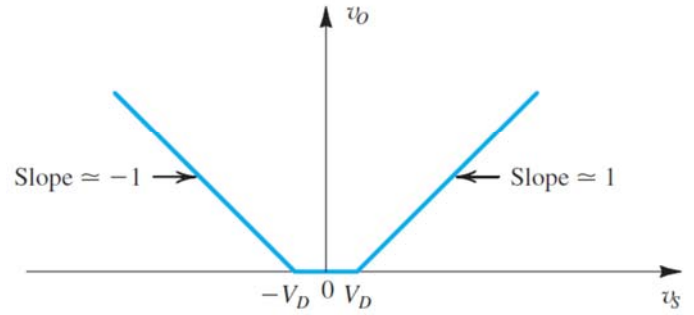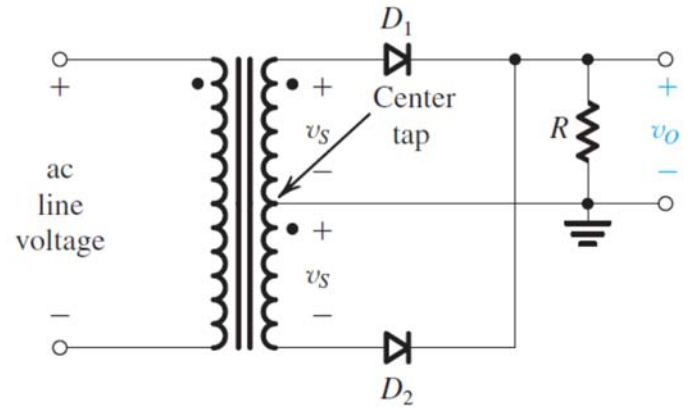
### The Full-Wave Rectifier:

The full-wave rectifier utilizes both halves of the input sinusoid. To provide a unipolar output, it inverts the negative halves of the sine wave.


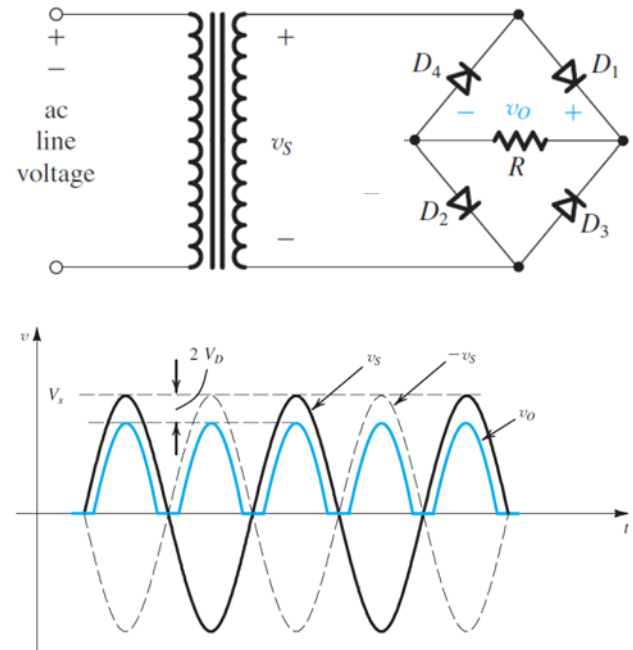
## The Bridge Rectifier:

- An alternative implementation of the full-wave rectifier.
- This circuit, known as the bridge rectifier because of the similarity of its configuration to that of the Wheatstone bridge, does not require a center-tapped transformer, a distinct advantage over the full-wave rectifier circuit.
- The bridge rectifier, however, requires four diodes as compared to two in the previous circuit.







## The bridge-rectifier circuit operates as follows:


- During the positive half-cycles of the input voltage,  $v_s$  is positive:
  - Thus current is conducted through diode  $D_1$ , resistor  $R$ , and diode  $D_2$ .
  - Meanwhile, diodes  $D_3$  and  $D_4$  will be reverse biased.
  - Observe that there are two diodes in series in the conduction path, and thus  $v_o$  will be lower than  $v_s$  by two diode drops (compared to one drop in the circuit previously discussed). *This is somewhat of a disadvantage of the bridge rectifier.*
- Next, consider the situation during the negative half-cycles of the input voltage:
  - The secondary voltage  $v_s$  will be negative, and thus  $-v_s$  will be positive, forcing current through  $D_3$ ,  $R$ , and  $D_4$ .
  - Meanwhile, diodes  $D_1$  and  $D_2$  will be reverse biased.
  - The important point to note, though, is that during both half-cycles, current flows through  $R$  in the same direction (from right to left), and thus  $v_o$  will always be positive.
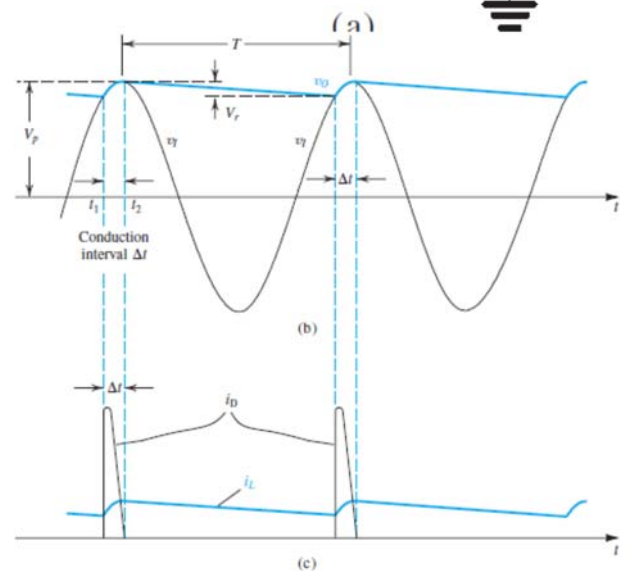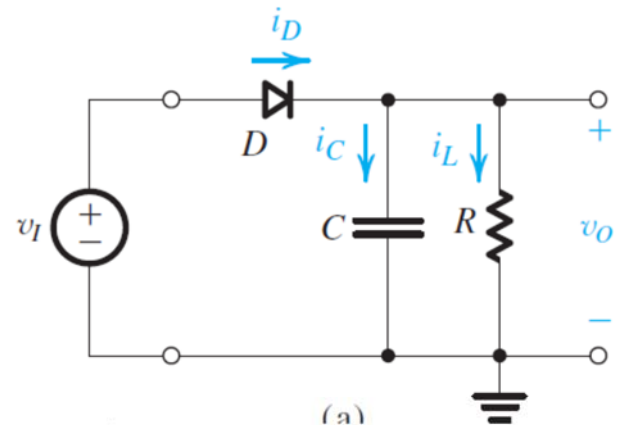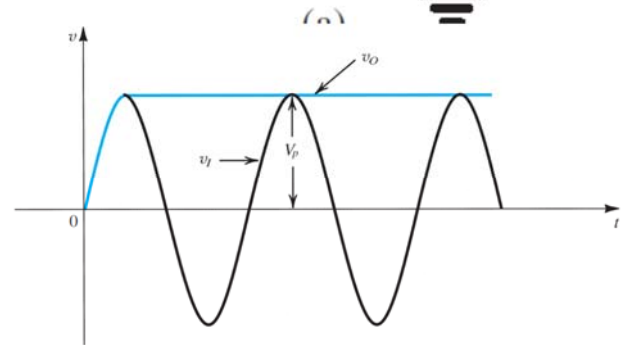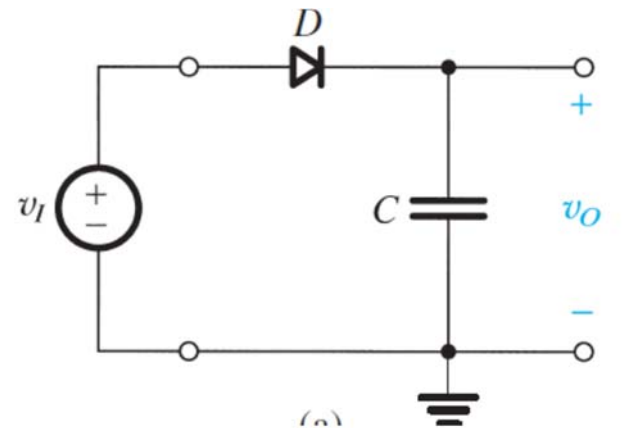
## The Rectifier with a Filter Capacitor—The Peak Rectifier:

The pulsating nature of the output voltage produced by the rectifier circuits discussed above makes it unsuitable as a dc supply for electronic circuits. A simple way to reduce the variation of the output voltage is to place a capacitor across the load resistor. It will be shown that this **filter capacitor** serves to reduce substantially the variations in the rectifier output voltage.




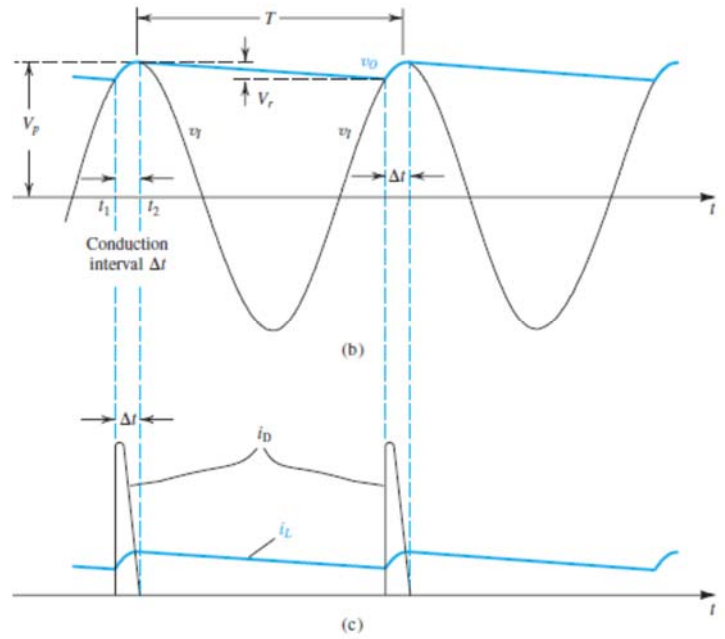
## Rectifier with a Filter Capacitor..Cont'd




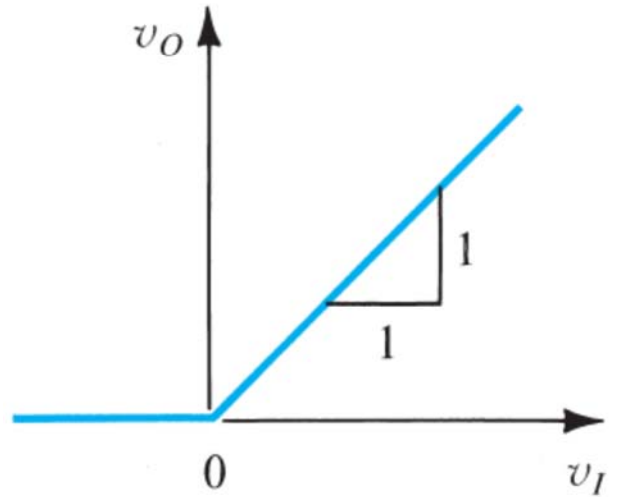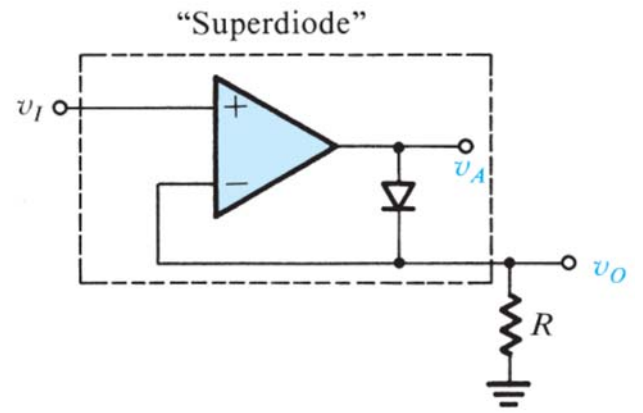
## Precision Half-Wave Rectifier - The Superdiode:



# Limiting and Clamping Circuits:

